


Electronic Trainer

Digital Electronics

Unit 1 - Fundamentals

Powering the Trainer

Power Switch

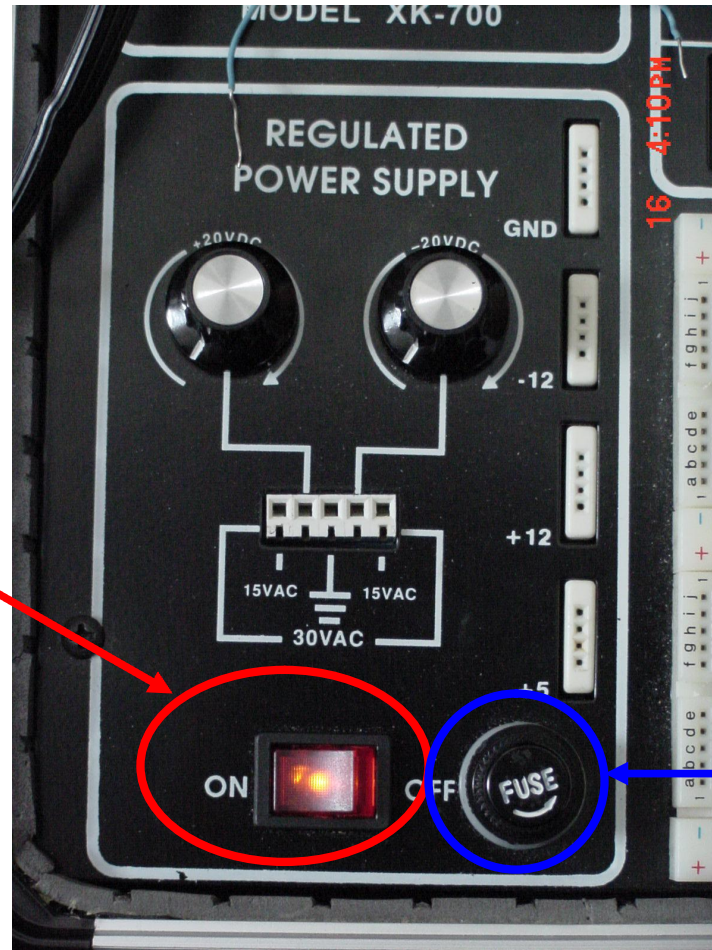

Fuse

Power Supply

Fixed Power Supply

Variable Power Supply



Power Supply

White Lines



Power Supply

AC Voltage
Connections



Power Supply



**+20 Volt
Variable
Connections**

Power Supply




**-20 Volt Variable
Connections**

Fixed Power Supply




Fixed Power
Supply


The Breadboard

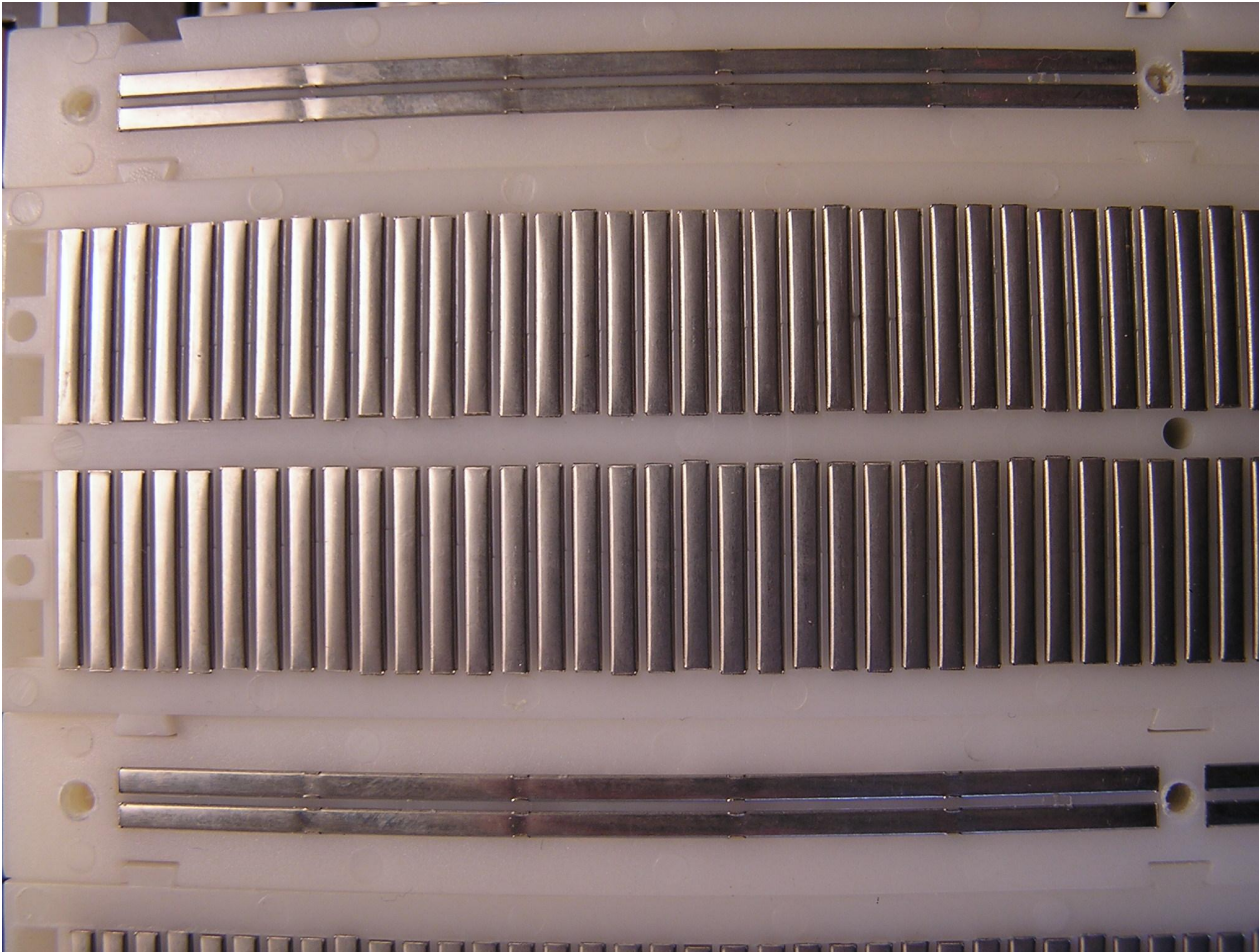


Horizontal Runs

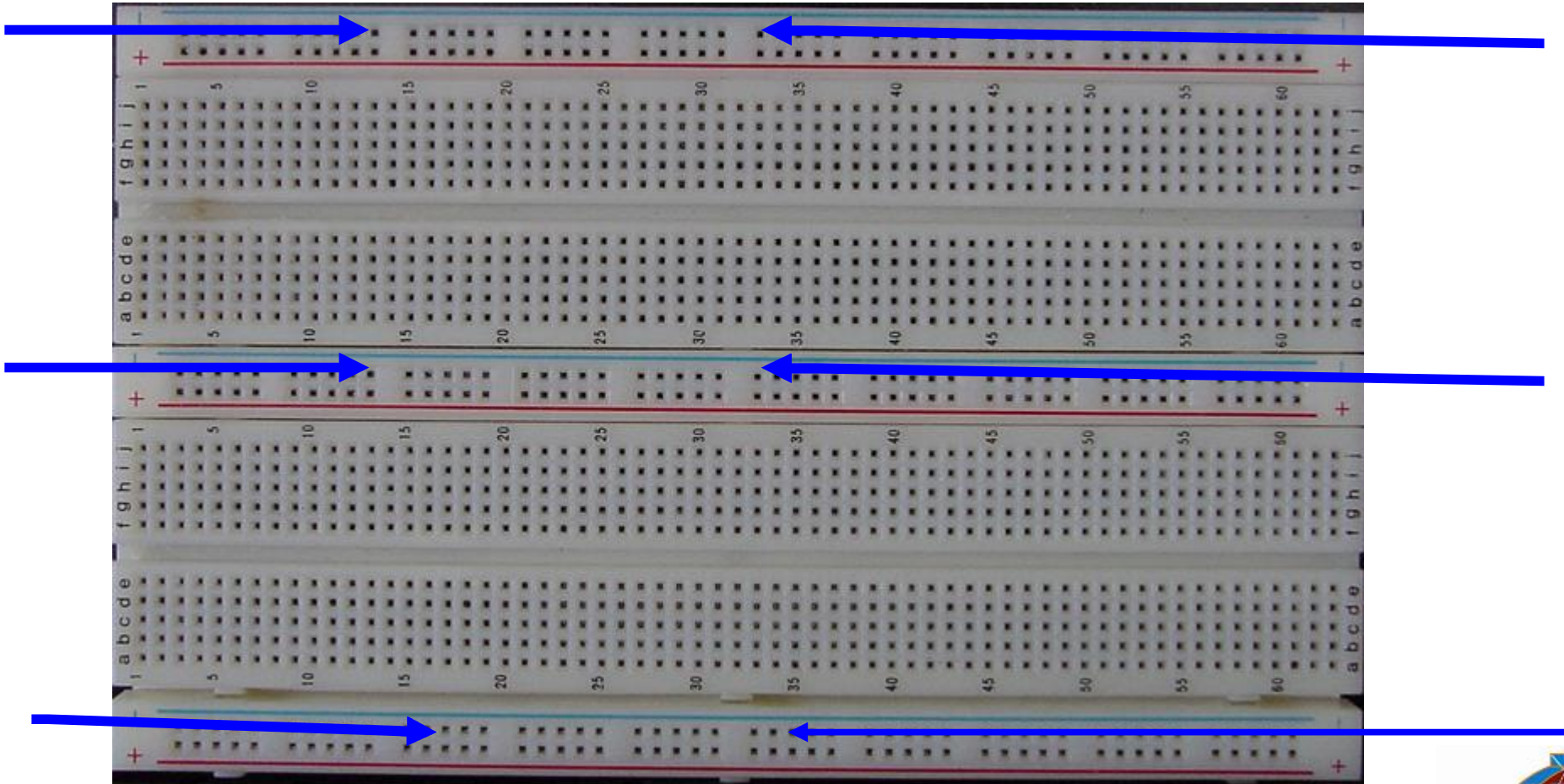

Horizontal Runs

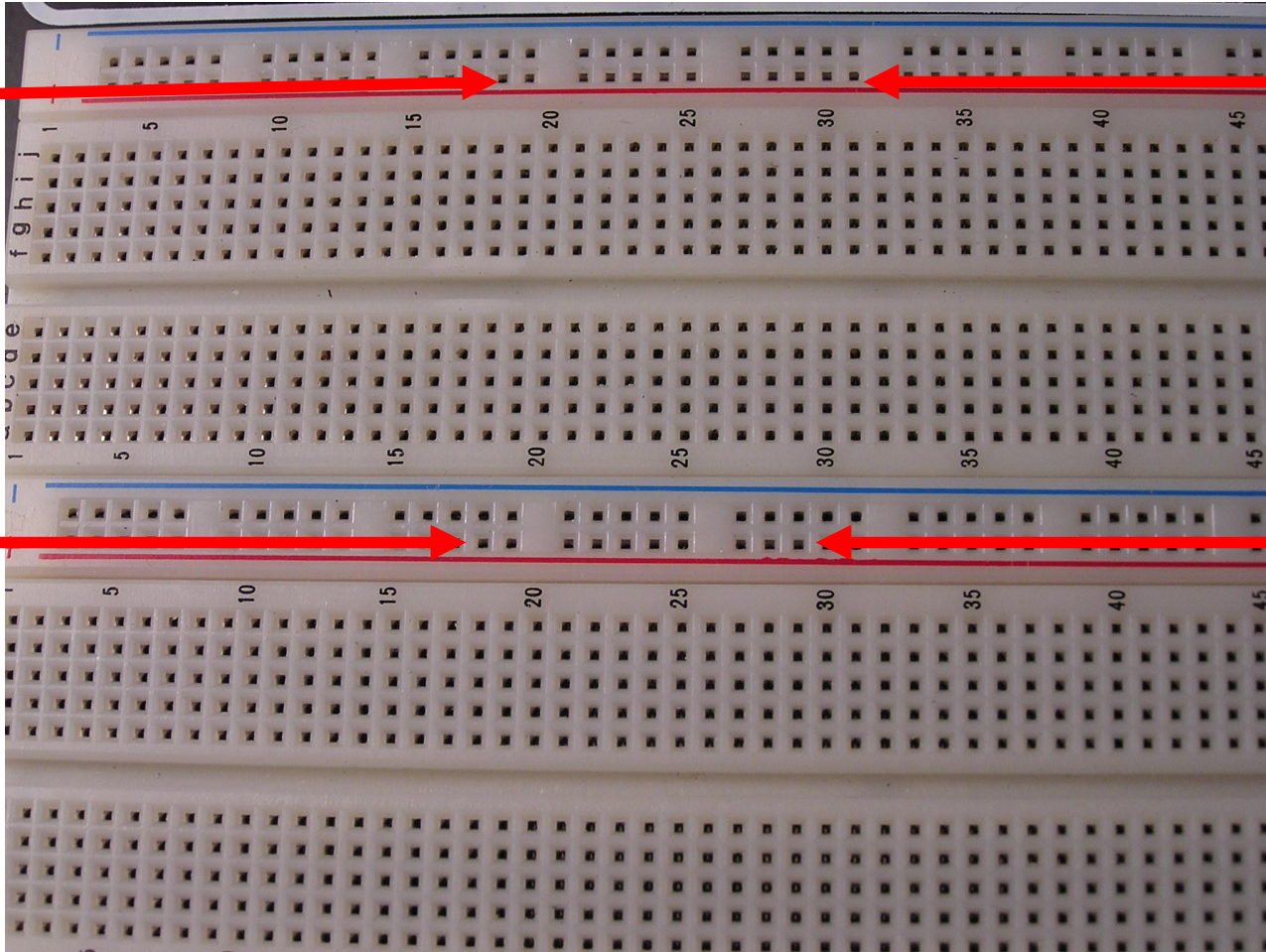


Using The Horizontal Holes

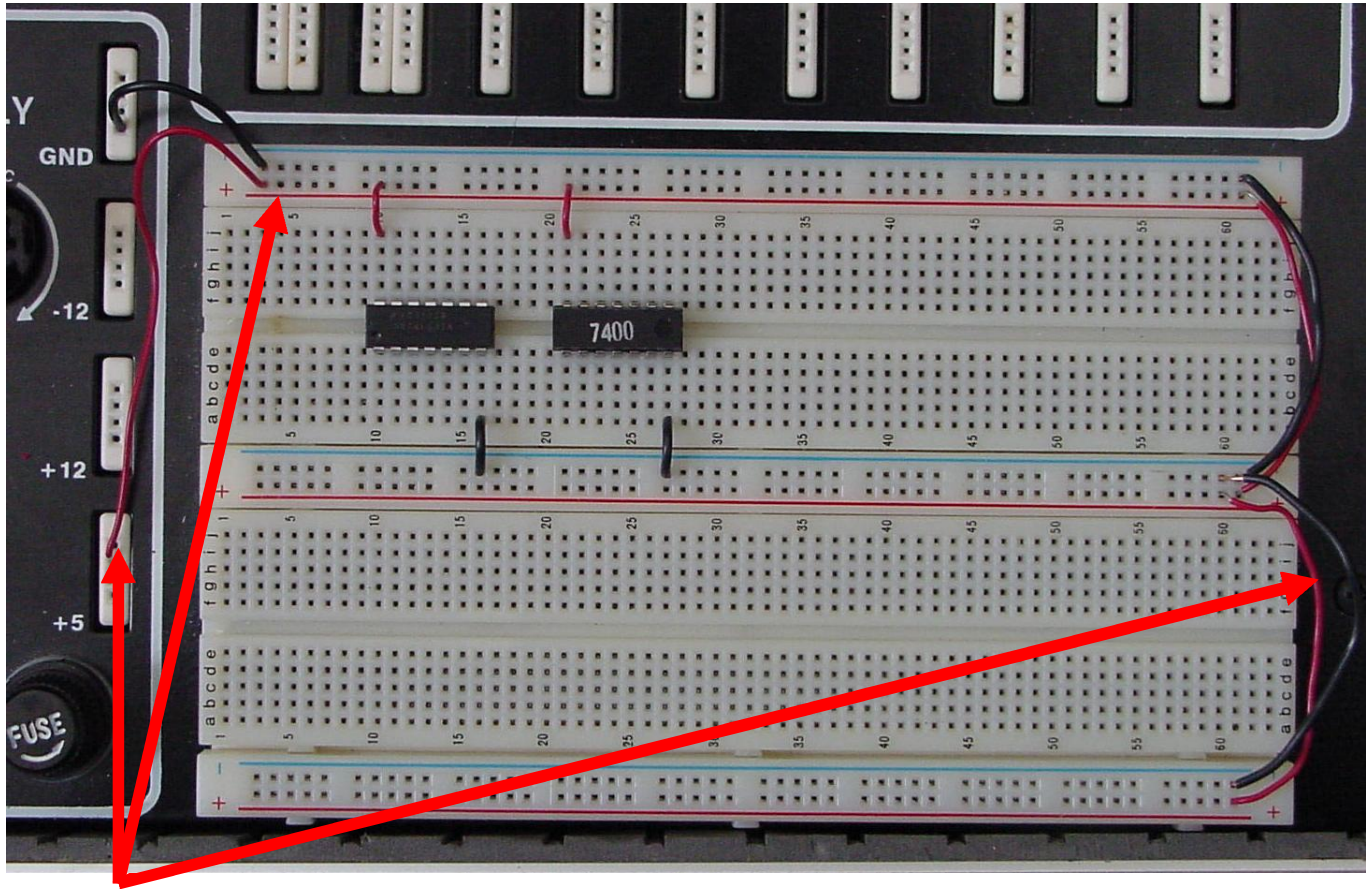


The Red marked holes and red wires are used for connecting the Voltage Source.

Using The Horizontal Holes

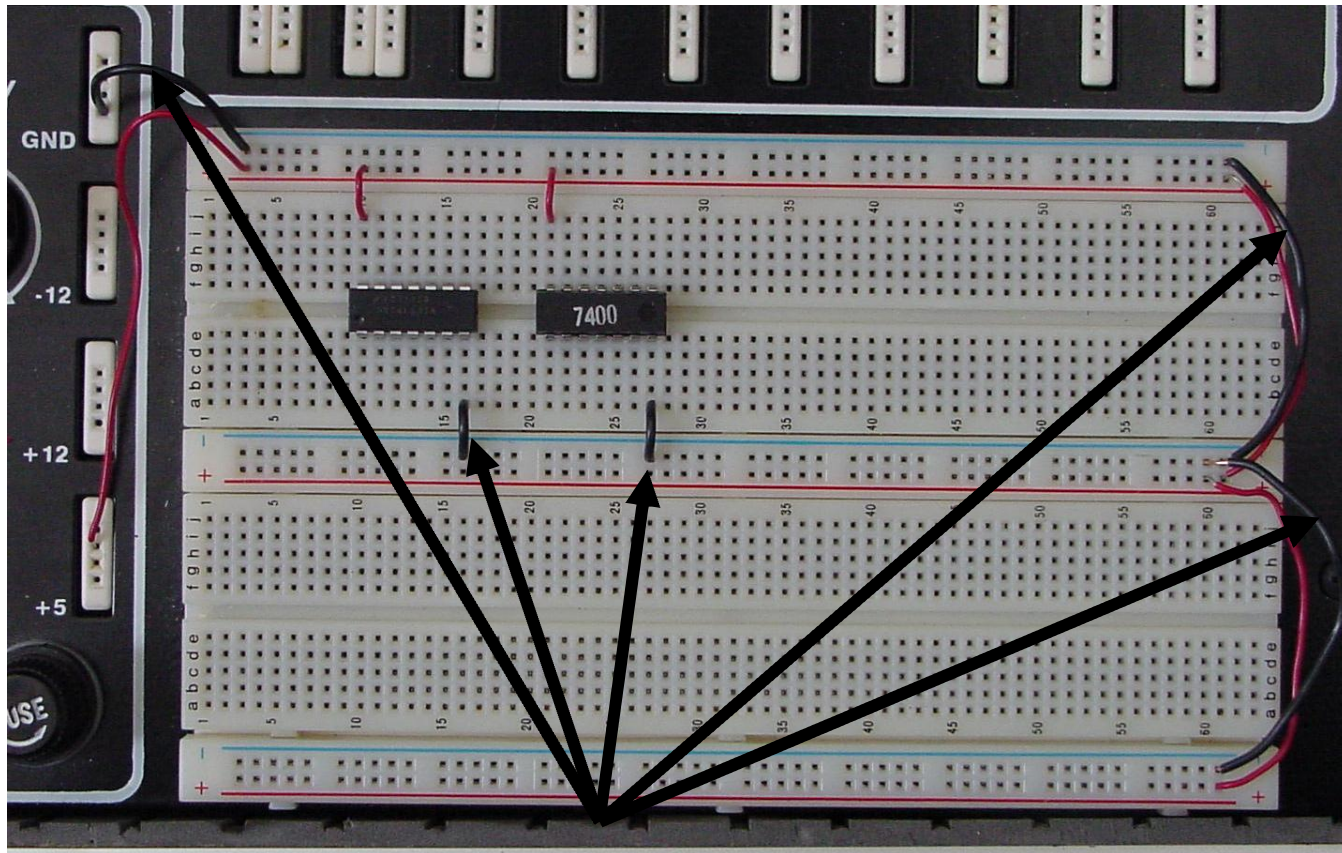


Grounds can be wired in the same way as the voltage sources, except black wires are used.

Vertical Runs

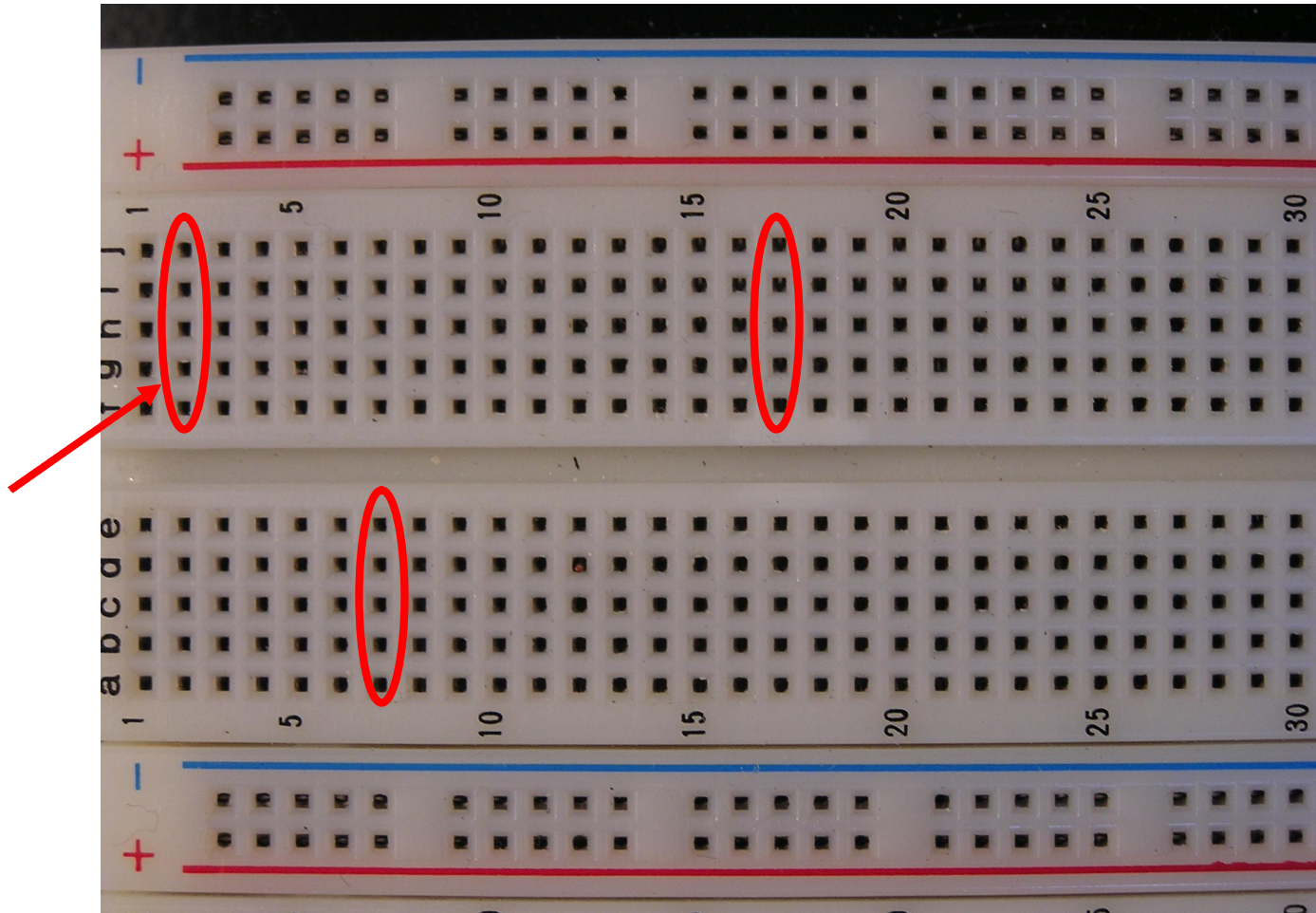


Vertical Runs

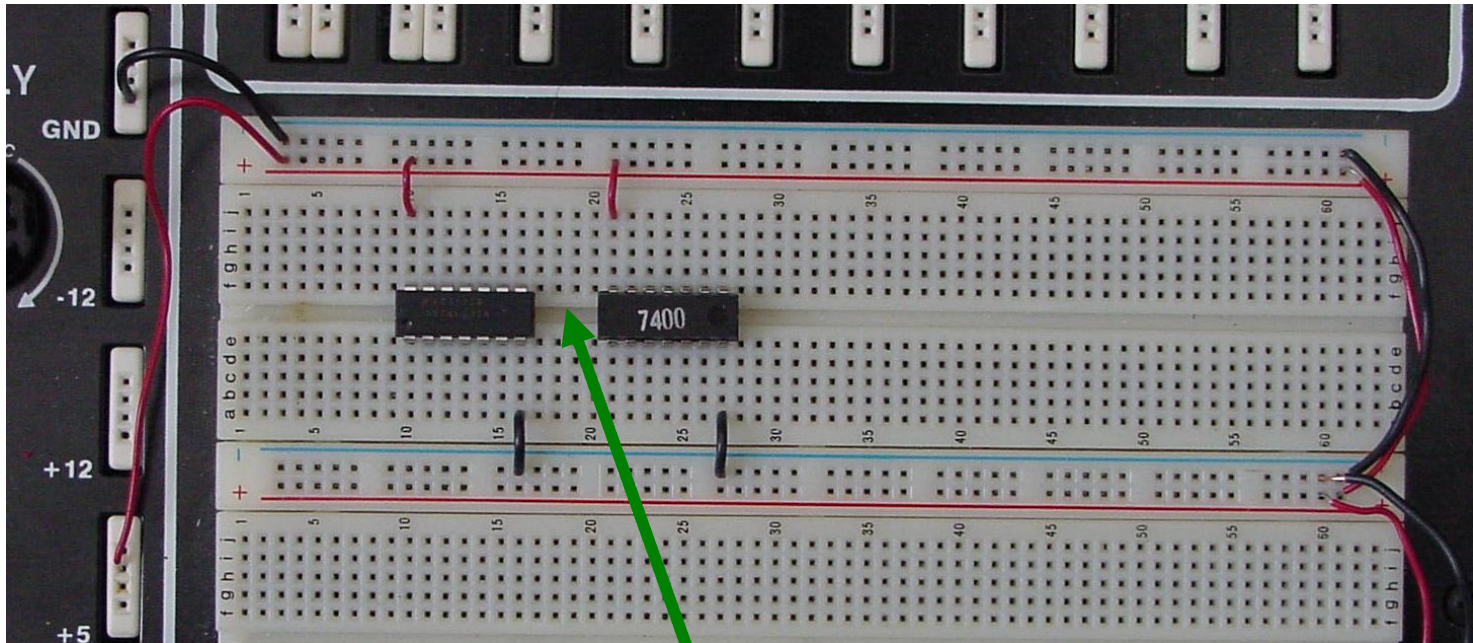


This gap the chip straddles separates the 5 pin run above the chip from the 5 pin run under it.

Connecting Horizontal and Vertical

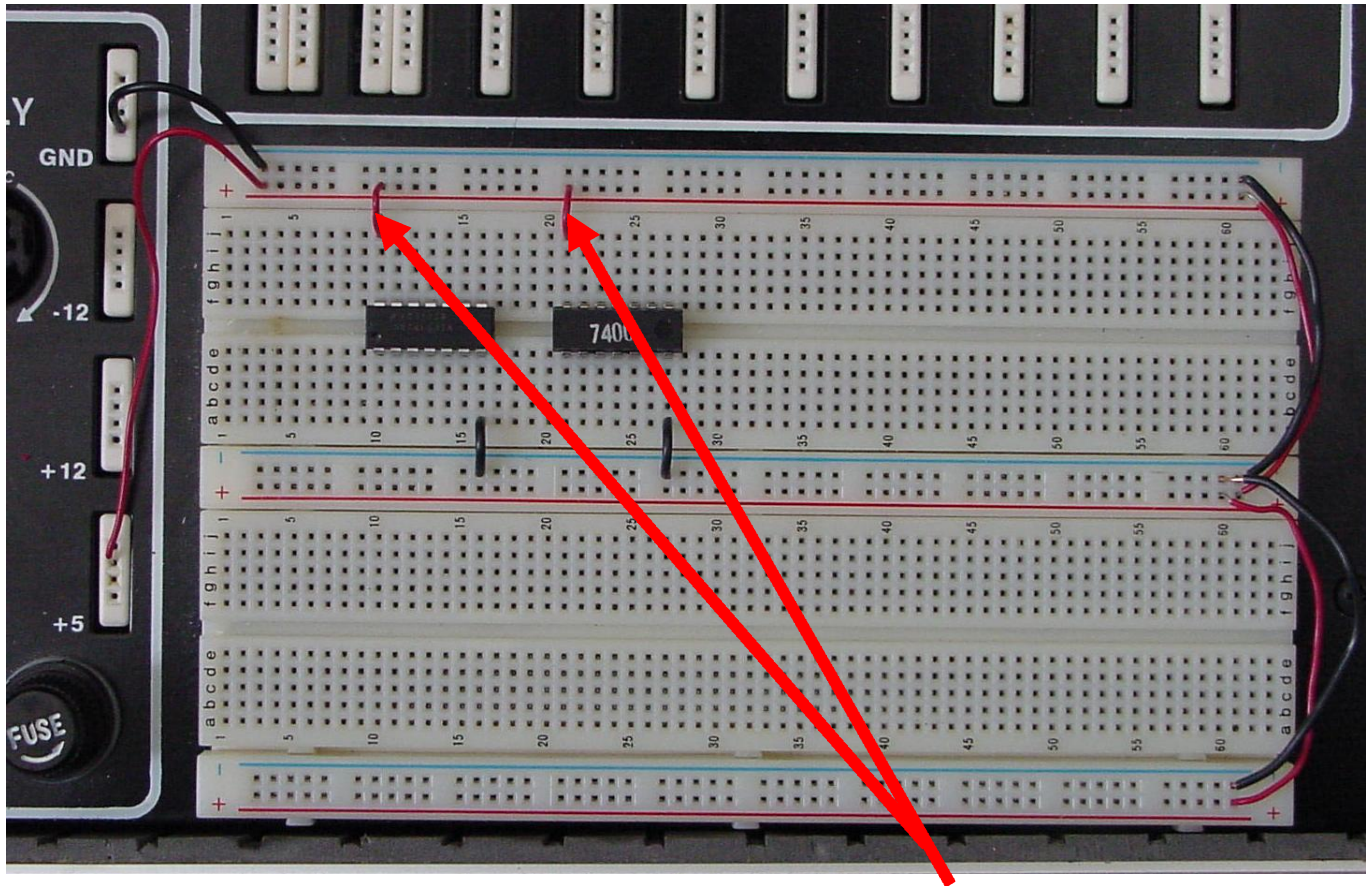

Electronic devices can be powered neatly and at any location from those power busses.


Simple Circuit, Ex. 1

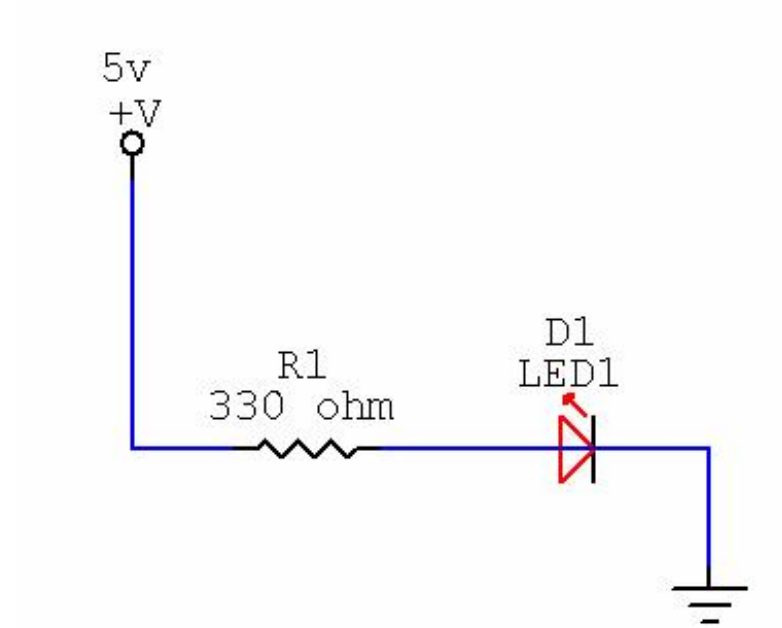

Schematic of Circuit, ex. 1


Example 1

Black Wire For Ground
End Of Circuit

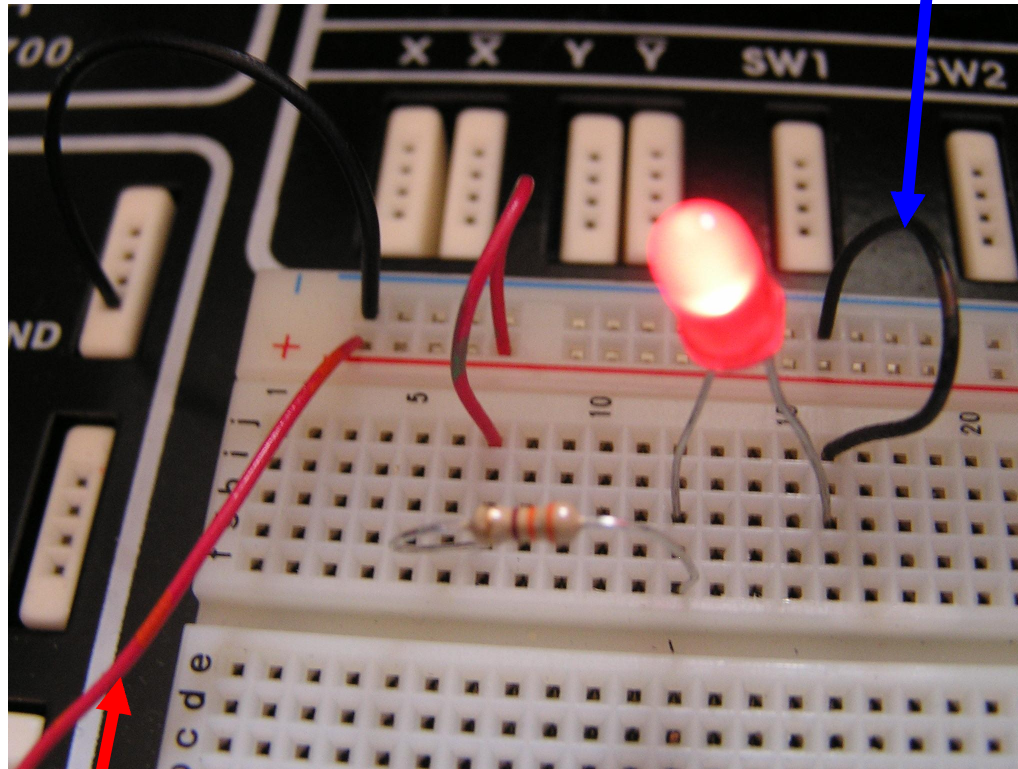


Red Wire For Source
End Of Circuit

Series Resistors, Ex. 2

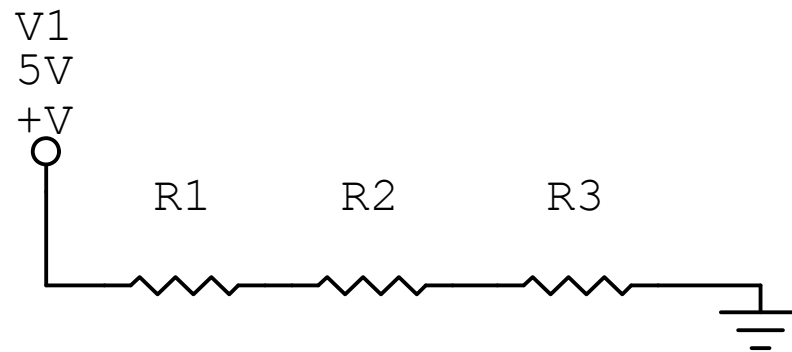


Schematic of Series circuit, ex. 2

Example 2 – Series Resistors

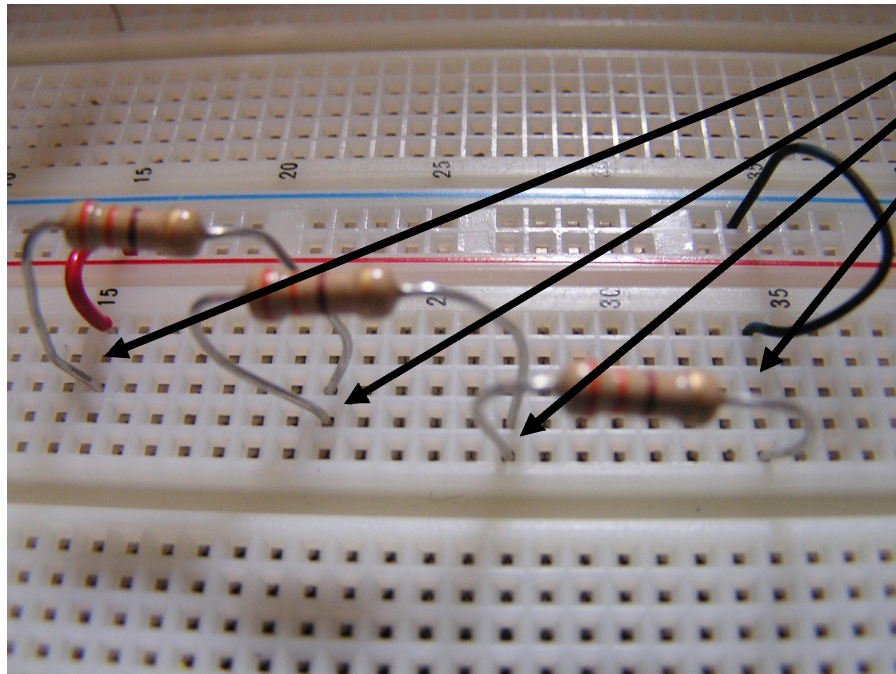


Notice how the ends of the resistors are placed in the group of five to connect them together in series.

Parallel Resistors, Ex. 3

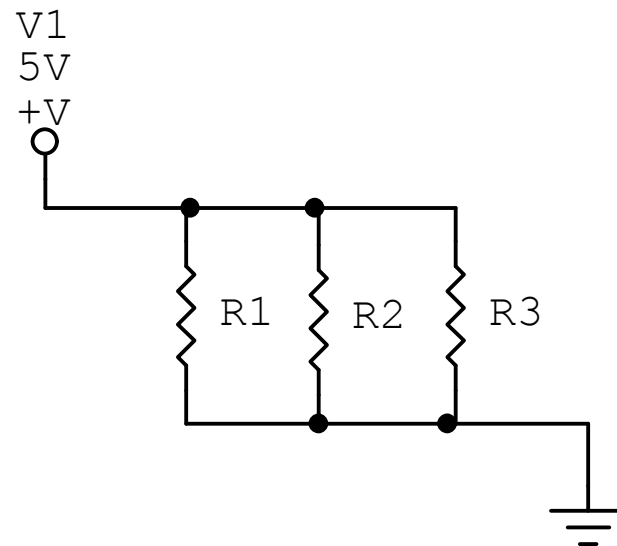


Schematic of Parallel circuit, ex. 3

Example 3, Parallel Resistors

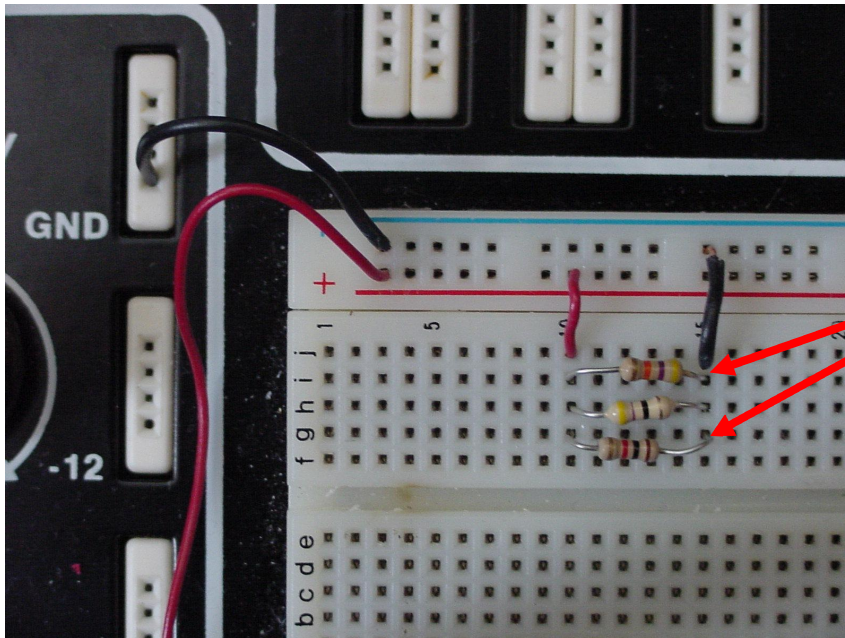


Note how the groups of five are used to create a parallel circuit.

Logic Switches

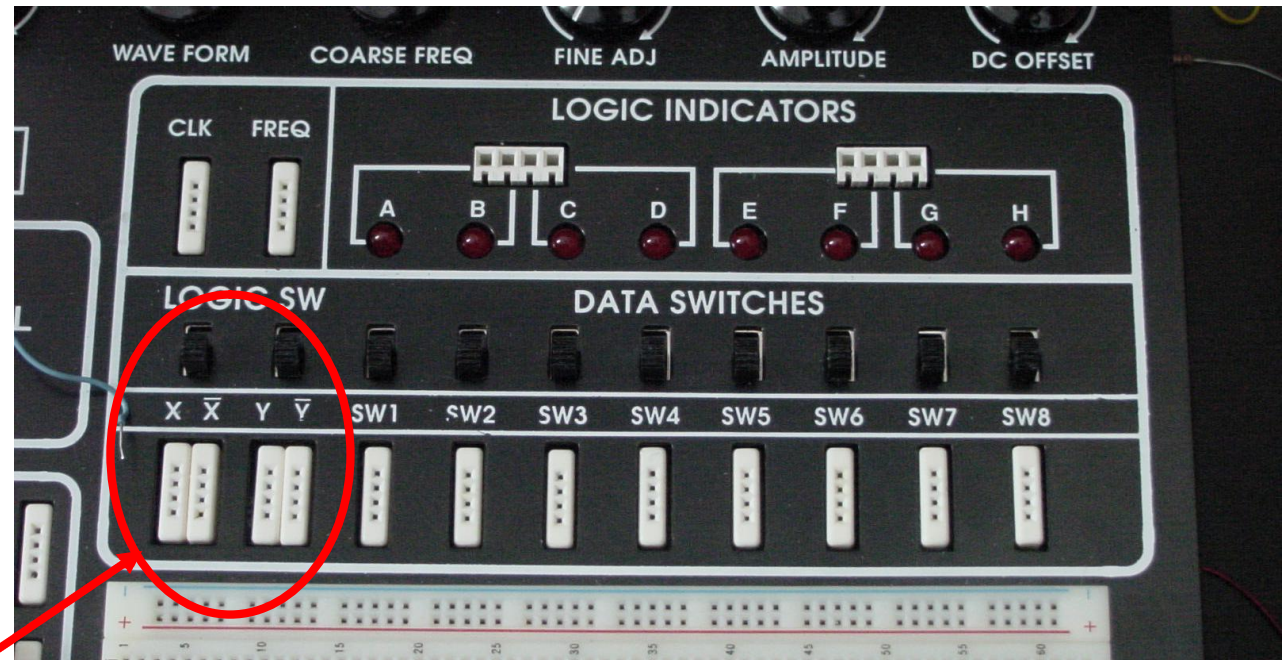

These logic switches have a set of four connections for a logic level and a set of four connections for the inverse.

Data Switches

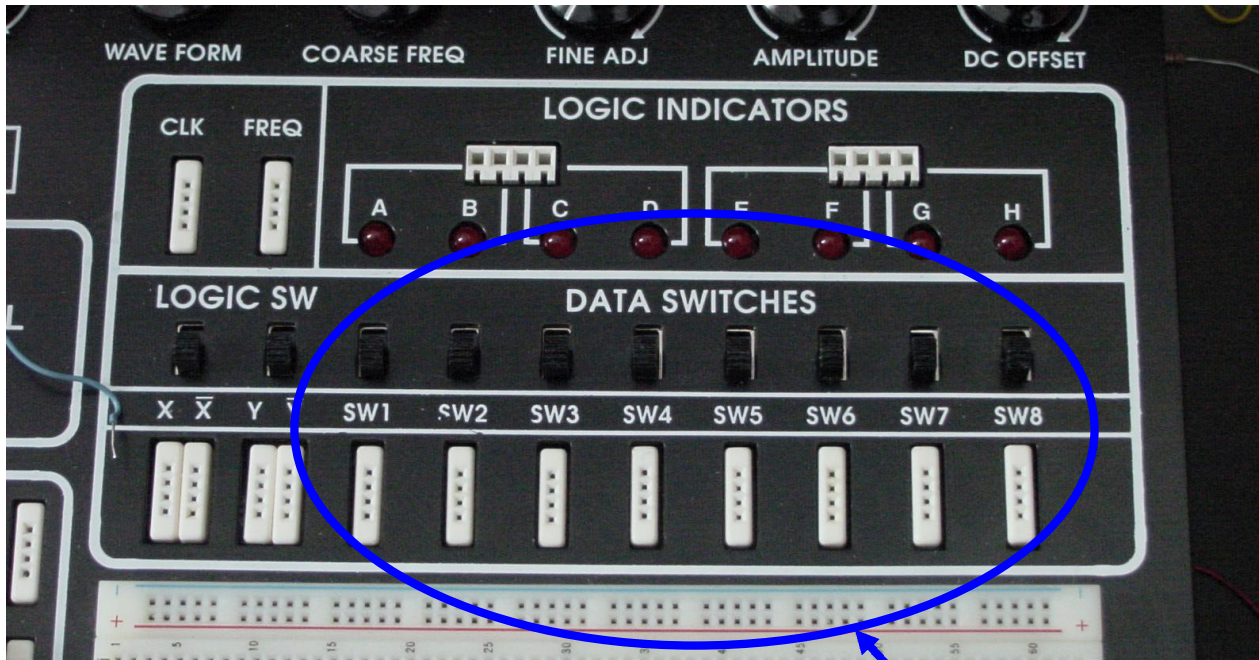


Data switches are used to switch an input from +5 volts to 0 volts. There are eight of them.

Logic Indicators




Logic Indicators are quick ways to connect an output to an LED to indicate high and low signals.

Using Logic Switch & Indicator

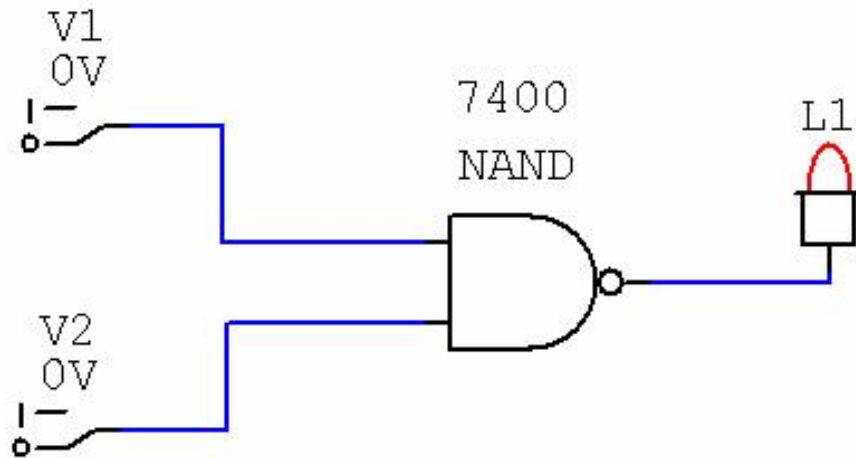

Schematic of NAND gate, ex. 4


Example 4

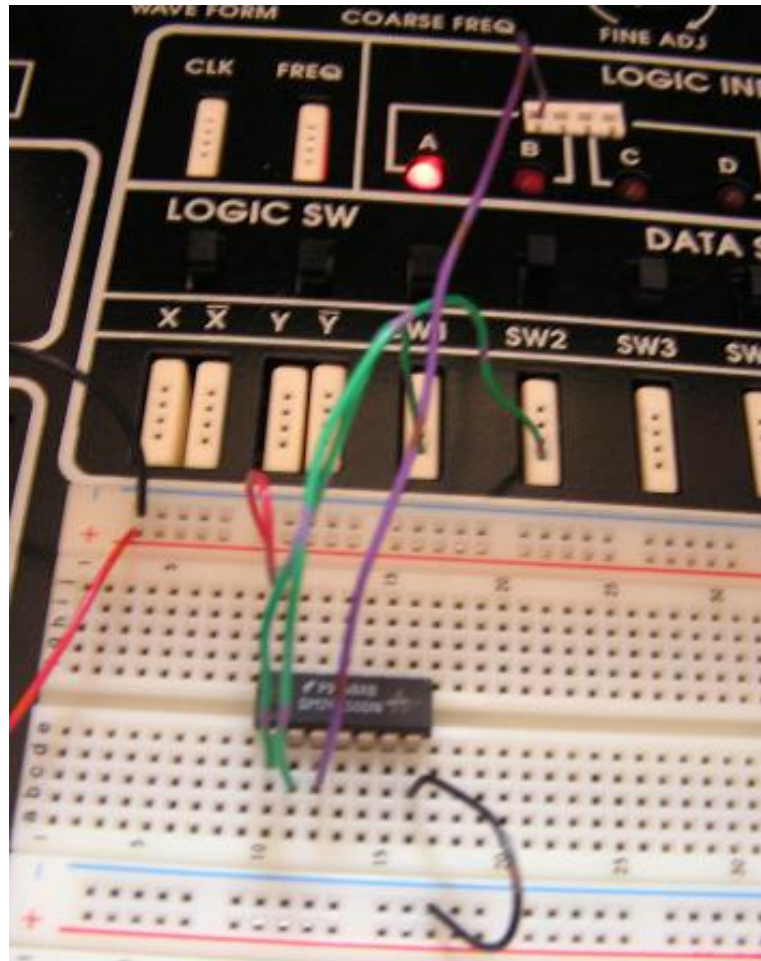

Truth Table NAND

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Frequency Generator

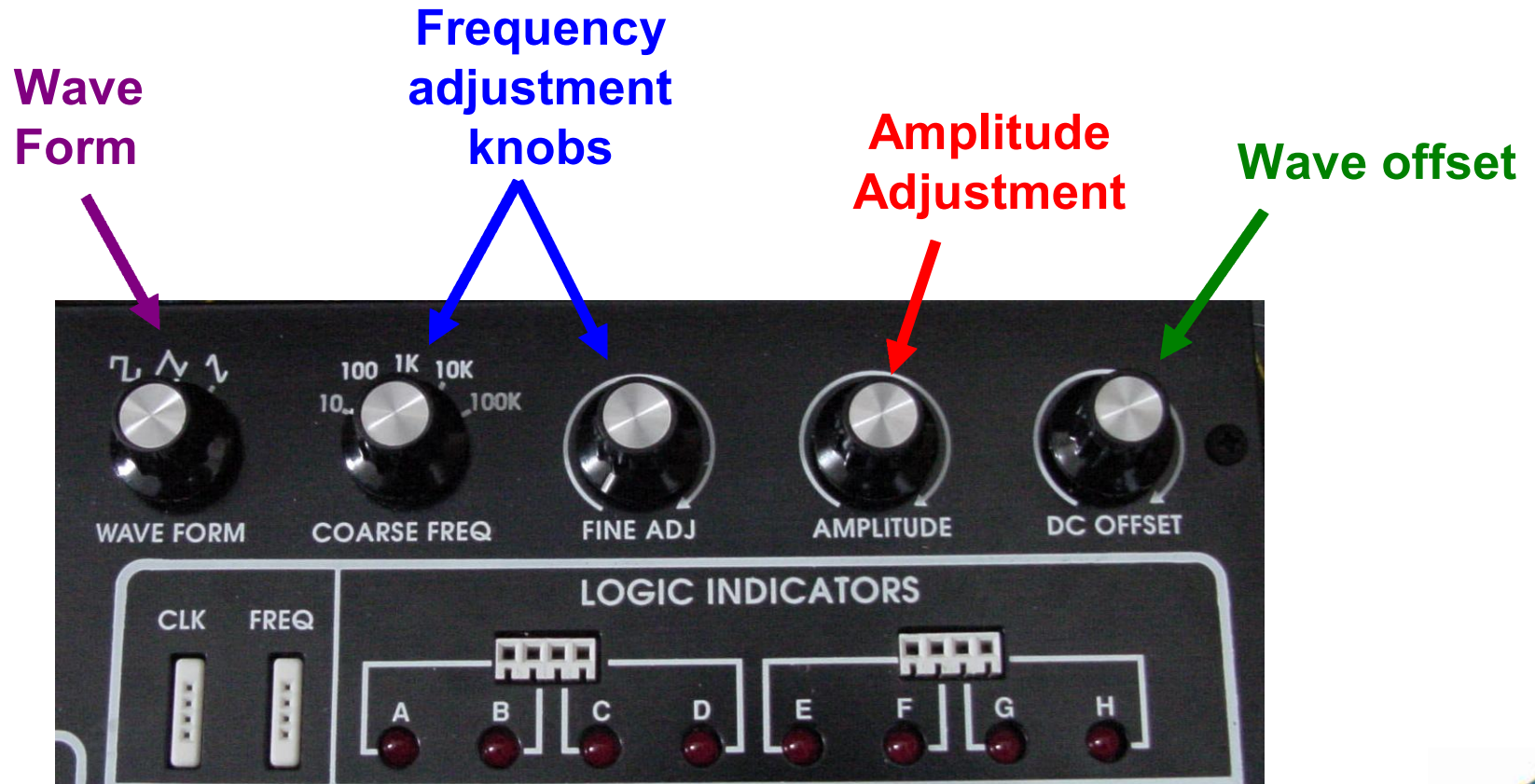

Frequency Generator



**Output Periodic
Square Wave only**

**Output Sine or Saw-
tooth Wave**

Curriculum Alignment:

Unit 1 - Fundamentals

Credits:

Writer: John Pierce

Content Editor: Donna E. Scribner

Narration: Donna E. Scribner

PLTW Editor: Ed Hughes

Production: CJ Amarosa

Video Production: CJ Amarosa

Audio: CJ Amarosa

Project Manager: Donna E. Scribner